

Basic Electrical Engineering

charge and current:

The relationship between current i , charge q and time t is

$$i = \frac{dq}{dt} \quad \text{--- (1)}$$

Integrating both side

$$q = \int_{t_0}^t i dt.$$

Voltage:

$$V = \frac{dw}{dq} \quad \text{--- (2)}$$

$$\text{Power: } P = \frac{w}{t}$$

$$= \frac{dw}{dt} \quad \text{--- (3)}$$

$$(1), (2), (3) \Rightarrow P = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = VI$$

$P = VI$

Practice problem:

Example: 1.4

$$i = 2A$$

$$t = 10s$$

The total charge,

$$\Delta q = I \Delta t$$

$$= 2 \times 10 = 20C.$$

The voltage drop,

$$V = \frac{dw}{dq} = \frac{2.3 \times 10^3}{20} = 115V.$$

$$V_{left} = -15V$$

$$V = \frac{dw}{dq}$$

$$= \frac{-30}{-6}$$

$$= 5V.$$

Example : 1.5

$$i = 5 \cos 60\pi t$$

$$(a) V = 3i \quad (b) V = 3 \frac{di}{dt}$$

(a) The voltage is $V = 3i$

$$= 3 \times 5 \cos 60\pi t$$

$$= 15 \cos 60\pi t$$

$$P = Vi$$

$$= 75 \cos^2 60\pi t$$

At, $t = 3 \text{ ms}$,

$$P = 75 \cos^2 (60\pi \times 3 \times 10^{-3})$$

$$= 53.48 \text{ W.}$$

$$\begin{aligned} & \text{At } t = 3 \text{ ms}, \\ & P = (-60\pi) 5 \sin 60\pi t \text{ W} \end{aligned}$$

(b) $V = 3 \frac{di}{dt}$

$$= 3(-60\pi) 5 \sin 60\pi t = -900\pi \sin 60\pi t \text{ V.}$$

$$P = Vi = -4500\pi \sin 60\pi t \cos 60\pi t \text{ W}$$

At, $t = 3 \text{ ms}$

$$P = -4500\pi \sin 0.18\pi \cos 0.18\pi \text{ W}$$

$$= -14137.167 \sin 32.4^\circ \cos 32.4^\circ$$

$$= -6.306 \text{ kW.}$$

Practice problem : 1.6

$$V = 240 \text{ V}$$

$$P = Vi = 240 \times 15 = 3600$$

$$i = 15 \text{ A}$$


$$P = \frac{dw}{dt}$$

$$dw = 60 \text{ kg}$$


$$t = ?$$

$$\Rightarrow dt = \frac{dw}{P} = \frac{6000}{3600}$$


$$= 16.667 \text{ s.}$$

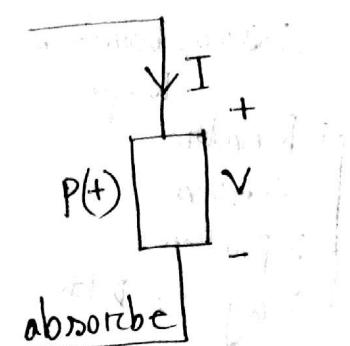

absorb

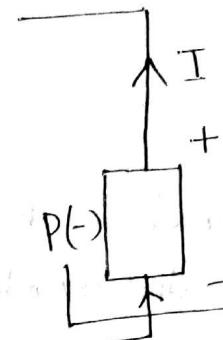

Supply

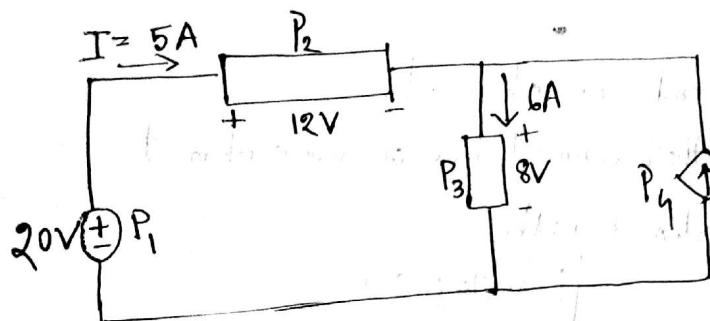

We know,

$$P = VI$$

$$P_1 = -VI$$

$$= (-20 \times 5)$$

$$= -100 \text{ W}$$

supplied power


$$P_2 = 12 \times 5 \\ = 60 \text{ W}$$

$$P_3 = 8 \times 5 \\ = 40 \text{ W}$$

$$P_4 = 8 \times (0.2 \times 5) \\ = -8 \text{ W}$$

$$\therefore P_1 + P_2 + P_3 + P_4 = -100 + 60 + 40 - 8 \\ \sum P = 0$$


Practise problem: 1.7

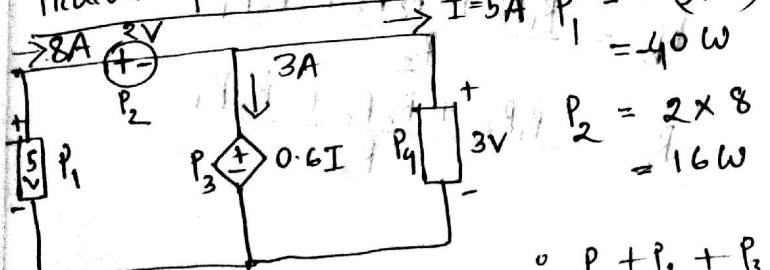


$$P_3 = 3 \times (0.6 \times 5) \\ = 9$$

$$P_4 = 3 \times 5 \\ = 15 \text{ W}$$
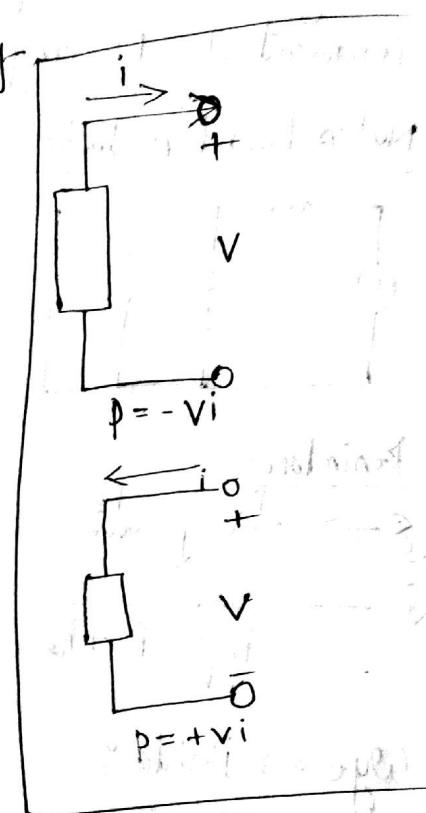
$$\therefore P_1 + P_2 + P_3 + P_4 = -40 + 16 + 9 + 15 \\ \therefore \sum P = 0$$




Ohm's law:

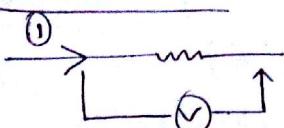

$$\forall x \in I \rightarrow v = IR$$

Voltage V , is directly proportional to the current I , flowing through the resistor.

Noden, brandhopen, loopp:

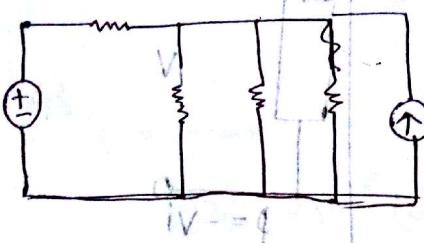


bimonthly → represent one settlement.

node → a point that connect two or more element


loop \rightarrow any closed path

~~Penindor:~~

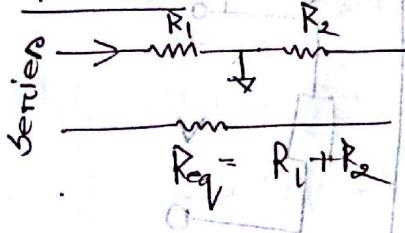

$$R_{\text{eq}} = R_1 + R_2$$

Wye \leftrightarrow Delta:

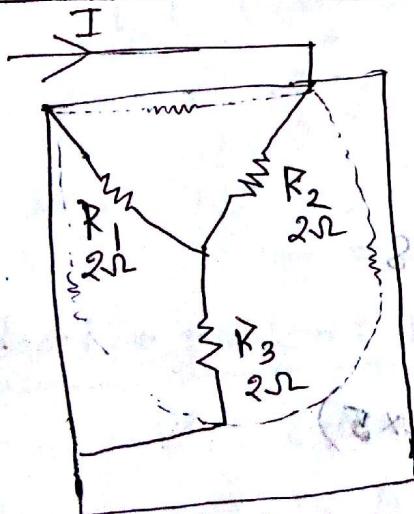

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

(2.2) \rightarrow ohm's law

(2.3) \rightarrow Nodots, branched loop pr

- \rightarrow Remindots
- \rightarrow Serien
- \rightarrow parallell
- \rightarrow Wye \leftrightarrow Delta.

$$\underline{RPLC: 2.1}$$

EVG & A.

$EV = \dots$

W A 901

WA 001 - 2
wbg katalog

卷之三

88 -

$$R_a = \frac{R_1 R_2 + R_2 R_3}{R_1}$$

Fit to your needs


$$D_1 = R_1 R_2 + R_1 R_3$$

$$R_2 = \frac{11.2}{P_2}$$


$$R_1 R_2 + R_3 R_4$$

$$R_c = \frac{M_1 z}{R_3}$$

8-19-00

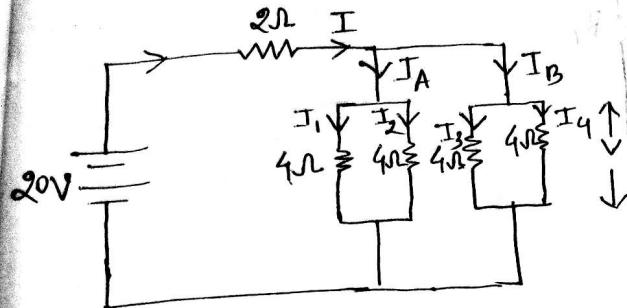

Current Divider Rule:

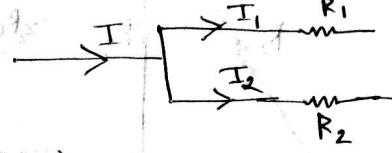


$$I_1 = \frac{R_2}{R_1 + R_2} \times I$$

$$V = IR \quad (V_1, \dots)$$

$$P = VI \quad I_2 = \frac{R_1}{R_1 + R_2} \times I$$

$$\hookrightarrow E = Pt$$

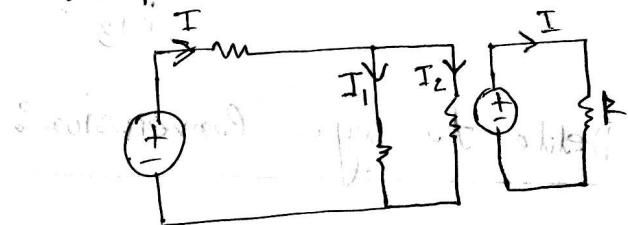

$$\frac{1}{R} = \frac{1}{4} + \frac{1}{4}$$

$$\frac{1}{R} = \frac{1}{2} \Rightarrow R = 2$$

$$\frac{1}{R} = \frac{1}{4} + \frac{1}{4}$$

$$\frac{1}{R} = \frac{1}{2} \Rightarrow R = 2$$

$$\frac{1}{R} = \frac{1}{2} + \frac{1}{2}$$

$$= 1$$

$$R = 2 + 1 = 3\Omega.$$

$$V = IR$$

$$I = \frac{V}{R} = \frac{20}{3} = 6.66$$

$$I_A = \left(\frac{2}{2+2} \right) 6.66$$

$$= 3.33$$

$$I_B = \left(\frac{2}{2+2} \right) \times 6.66$$

$$= 3.33$$

$$I_1 = \left(\frac{2}{2+2} \right) \times 3.33$$


$$= 1.665$$

$$I_2 = \left(\frac{2}{2+2} \right) \times 3.33$$

$$= 1.665$$

CT \Rightarrow প্রমাণ (পর্যবেক্ষণ করা) Wye Δ

$$(2.5 - 17)$$

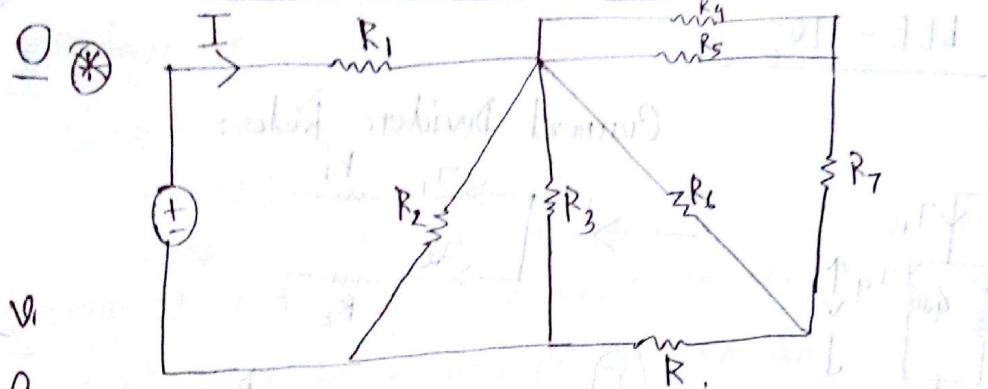

$$\frac{1}{R_8} = \frac{1}{R_4} + \frac{1}{R_5} \rightarrow B$$

$$R_9 = R_8 + R_7$$





$$\frac{1}{R_{10}} = \frac{1}{R_9} + \frac{1}{R_6}$$

$$\frac{1}{R_{11}} = \frac{1}{R} + \frac{1}{R_{10}}$$

$$\frac{1}{R_{12}} = \frac{1}{R_{11}} + \frac{1}{R_3} + \frac{1}{R_2}$$

$$R_{13} = R_{12} + R_1$$

Delta to wye Conversion

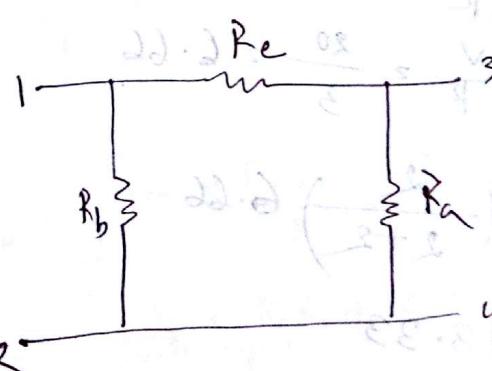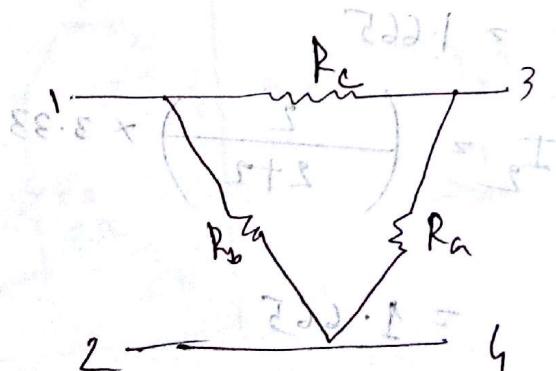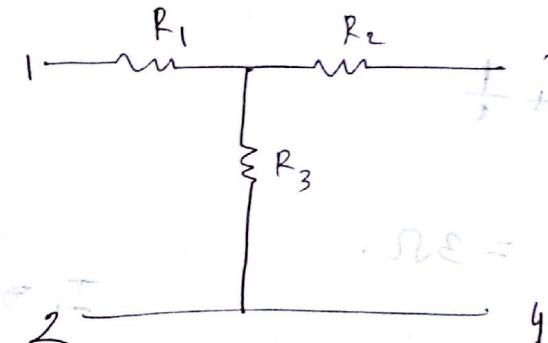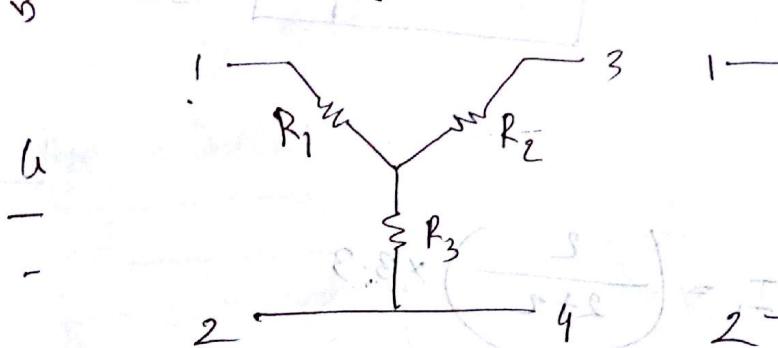

$$R_{12}(Y) = R_1 + R_3$$

$$R_{12}(A) = R_1 || (R_a + R_c)$$

$$R_{12} = R_1 + R_3 = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c} \quad \textcircled{1}$$

Similarly:

$$R_{13} = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c}$$

$$R_{13} = R_1 + R_2 = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c} \quad \textcircled{2}$$

$$R_{34} = R_2 + R_3 = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c} \quad \textcircled{3}$$

$$\textcircled{1} - \textcircled{3} \Rightarrow$$

$$R_1 - R_2 = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c} - \frac{R_a(R_b + R_c)}{R_a + R_b + R_c}$$

$$R_1 - R_2 = \frac{R_b R_a + R_b R_c - R_a R_b - R_a R_c}{R_a + R_b + R_c}$$

$$R_1 - R_2 = \frac{R_c(R_b - R_a)}{R_a + R_b + R_c} \quad \textcircled{4}$$

$$\textcircled{2} + \textcircled{4} \Rightarrow$$

$$2R_1 = \frac{\cancel{R_a R_b + R_b R_c}}{R_a + R_b + R_c} + \frac{\cancel{R_b R_c - R_a R_c}}{R_a + R_b + R_c}$$

$$2R_1 = \frac{R_a R_c + R_b R_c + R_b R_c - R_a R_c}{R_a + R_b + R_c}$$

$$2R_1 = \frac{R_a R_c + R_b R_c + R_b R_c - R_a R_c}{R_a + R_b + R_c}$$

$$2R_1 = \frac{2R_b R_c}{R_a + R_b + R_c}$$

$$C \quad R_1 = \frac{R_b R_c}{R_a + R_b + R_c} - ⑤$$

(1) \rightarrow
 (2) \rightarrow

$$R_1 + R_2 - R_1 + R_2 = \frac{R_a R_c + R_b R_c}{R_a + R_b + R_c} - \frac{R_b R_c - R_a R_c}{R_a + R_b + R_c}$$

$$V \quad ⑦ 2R_2 = \frac{R_a R_c + R_b R_c - R_b R_c + R_a R_c}{R_a + R_b + R_c}$$

$$N \quad ⑧ 2R_2 = \frac{2R_a R_c}{R_a + R_b + R_c}$$

$$C \quad ⑨ R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

① - ⑤

$$R_1 + R_3 - R_1 = \frac{R_a R_b + R_b R_c}{R_a + R_b + R_c} - \frac{R_b R_c}{R_a + R_b + R_c}$$

$$= \frac{R_a R_b + R_b R_c - R_b R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$


wye to Delta :

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} - ①$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} - ②$$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_a R_b R_c (R_a + R_b + R_c)}{(R_a + R_b + R_c)^2}$$
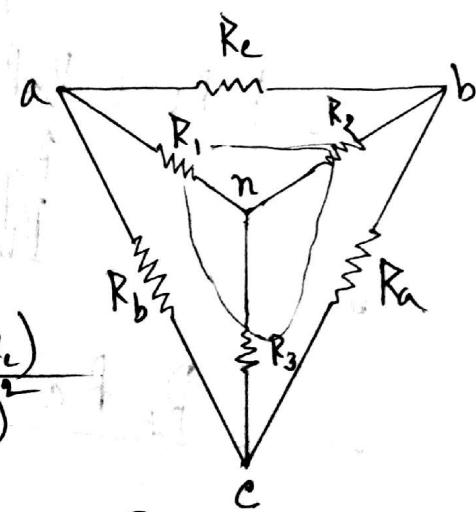
$$= \frac{R_a R_b R_c}{R_a + R_b + R_c} - ③$$



Dividing eqⁿ ③ by each of eqⁿ ① to ③ leads to the following eqⁿ.

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

Example
2.14
D - Y



(a)

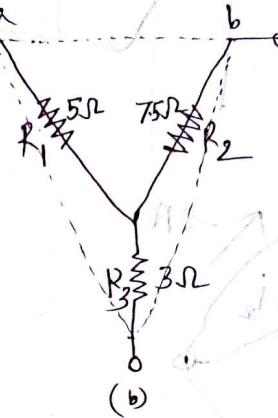


(b)

$$R_1 = \frac{10 \times 25}{15 + 10 + 25} = \frac{250}{50} = 5\Omega$$

$$R_2 = \frac{25 \times 15}{15 + 10 + 25} = \frac{375}{50} = 7.5\Omega$$

$$R_3 = \frac{10 \times 15}{15 + 10 + 25} = \frac{150}{50} = 3\Omega$$

Practice problem: 2.14

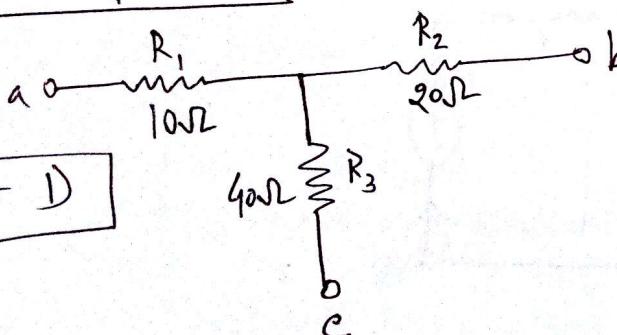

Y - D




$$R_a = \frac{10 \times 20 + 20 \times 40 + 40 \times 10}{10} = 140\Omega$$

$$R_b = \frac{10 \times 20 + 20 \times 40 + 40 \times 10}{20} = 70\Omega$$

$$R_c = \frac{10 \times 20 + 20 \times 40 + 40 \times 10}{40} = 35\Omega$$

KVL and KCL

KCL:

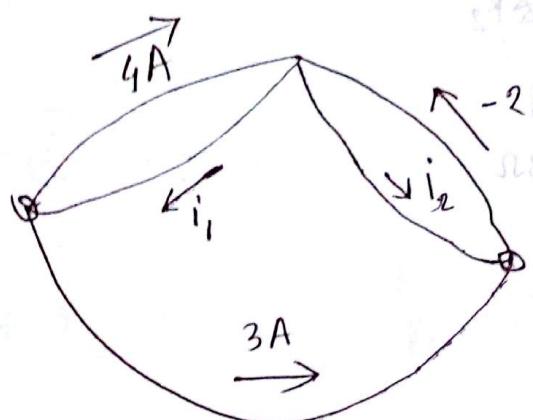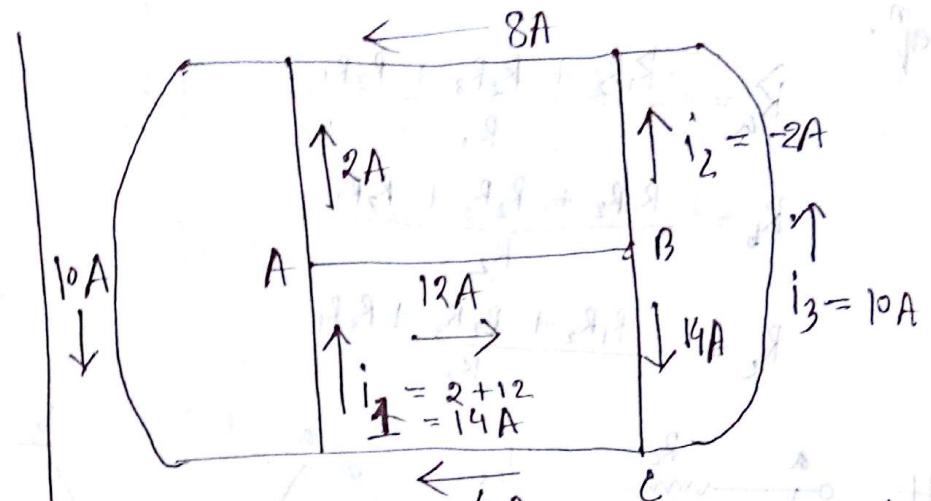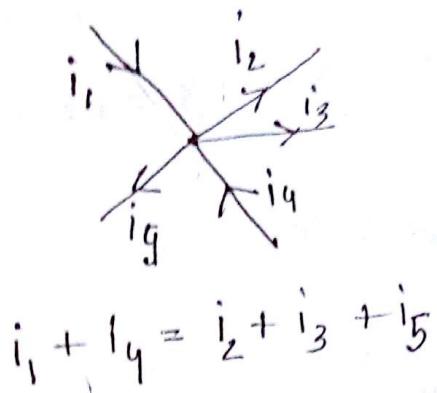

$$\text{Slope} = \frac{0.1 \times 0.01 + 0.2 \times 0.02 + 0.3 \times 0.03}{0.1} = 8$$


$$\text{Slope} = 0.1 \times 0.01 + 0.2 \times 0.02 + 0.3 \times 0.03 = 8$$

$$0.1 \times 0.01 + 0.2 \times 0.02 + 0.3 \times 0.03 = 8$$

KVL: Total voltage since = total voltage drop around loop path.


→ around an closed loop path.

$$V_1, V_2, V_3 = ?$$

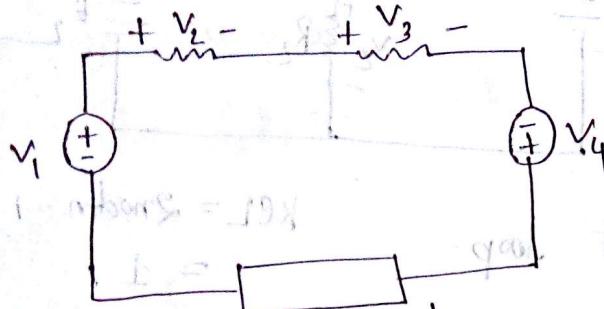

$$\text{KVL} \Rightarrow V_1 + V_4 = V_2 + V_3 + V_5$$

$$+V_1 - V_2 - V_3 + V_4 - V_5 = 0$$

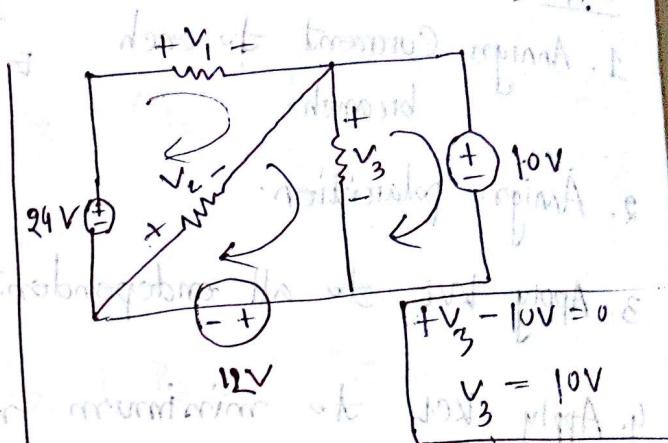

$$-V_2 - V_3 - 12V = 0$$

$$-V_2 - 10 - 12 = 0$$


$$V_2 = -22V$$

$$+24V - V_1 + V_2 = 0$$

$$24 - V_1 - 22 = 0$$

$$V_1 = -2V$$

Branch Current Analysis

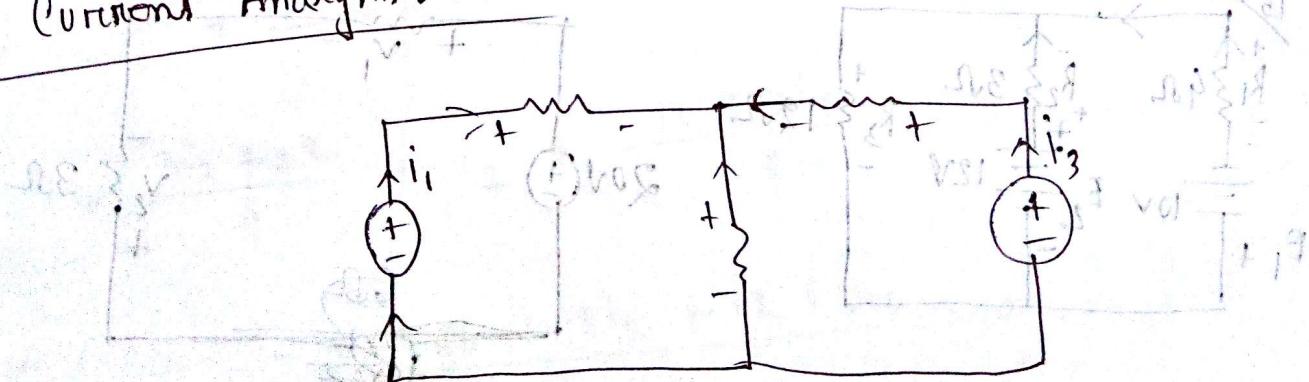


Branche current Analyzing

$$KCL \Rightarrow I_1 + I_3 = I_2$$

Step:

1. Assign Current to each branch.

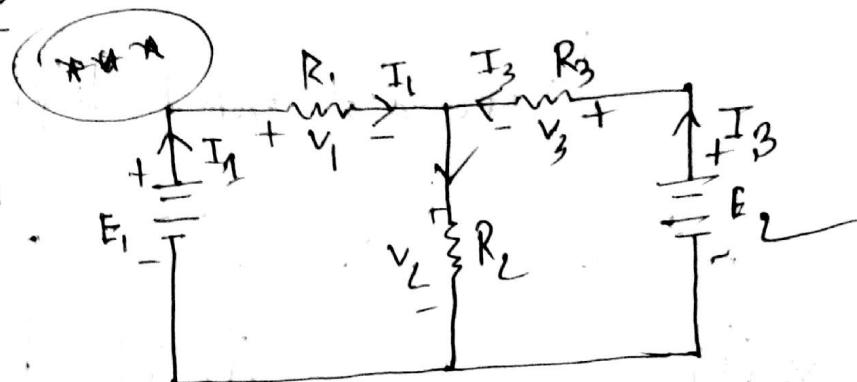

2. Assign polarities.


3. Apply KVL to all independent loop.

$$\begin{aligned} KVL &= 2 \text{ noden} - 1 \\ &= 1 \end{aligned}$$


4. Apply KCL to minimum numbers of noden.

5. Solve all equation


Example: 2.8

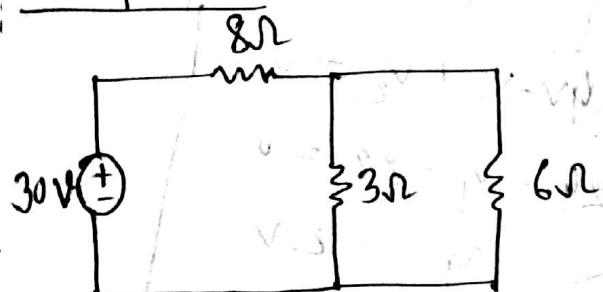


Boykentend

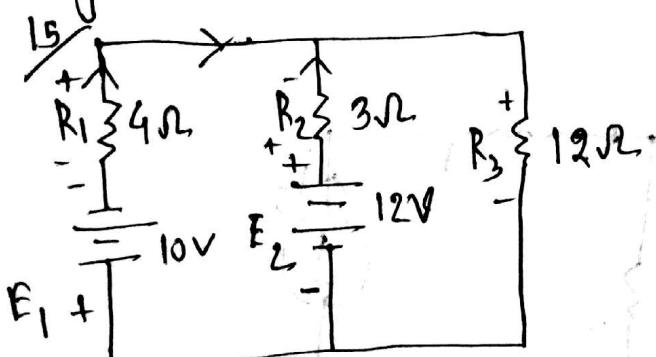

Example: 2.6

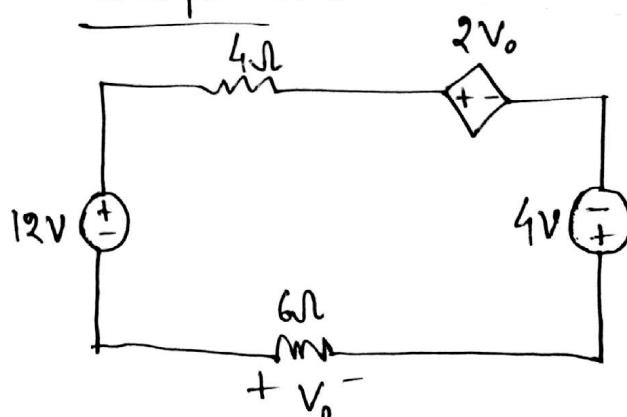

Example: 2.5

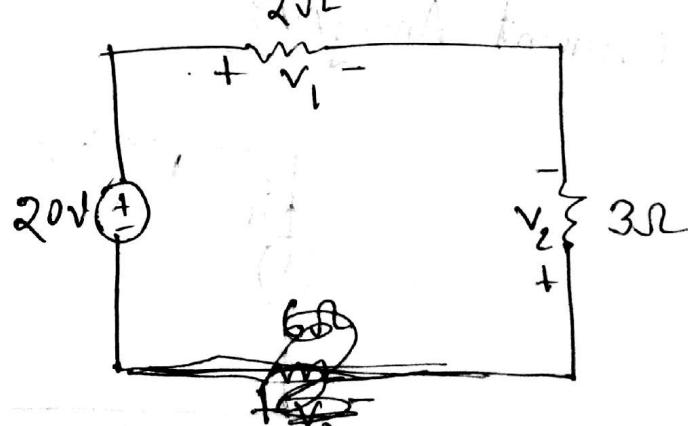

(1) (2) (3)

$$KCL \Rightarrow I_1 + I_3 = I_2 \quad I_1 - I_2 + I_3 = 0$$

KVL \Rightarrow ①

$$+E_1 - V_1 - V_1 = 0$$

$$E_1 - i_1 R_1 - i_2 R_2 = 0$$

$$(1-3)i_2 + 3i_3 = E_1 \\ -R_1 i_1 - R_2 i_2 + 0i_3 = -E_1$$

KVL \Rightarrow ②

$$V_2 + V_3 - E_2 = 0$$

$$i_2 R_2 + i_3 R_3 - E_2 = 0$$

$$0i_1 + R_2 i_2 + R_3 i_3 = E_2$$

Boujanted:

$$-i_1 + i_2 + i_3 = 0$$

$$-10 + 4i_1 - 3i_2 - 12 = 0$$

$$12 - 3i_2 - 12i_3 = 0$$

$$-12i_3 = -12 - 3i_2$$

$$\Rightarrow -12i_3 = -(12 + 3i_2)$$

$$\Rightarrow i_3 = \frac{12 + 3i_2}{12}$$

$$\Rightarrow -22 + 4i_1 - 3i_2 = 0$$

$$\Rightarrow 4i_1 = 3i_2 + 22$$

$$\Rightarrow i_1 = \frac{3i_2 + 22}{4}$$

$$-\frac{3i_2 + 22}{4} + i_2 + \frac{12 + 3i_2}{12} = 0$$

$$\Rightarrow \frac{-9i_2 + 66 + 12i_2 + 12 + 3i_2}{12} = 0$$

$$\Rightarrow \frac{6i_2 + 78}{12} = 0$$

$$i_2 = -\frac{78}{6}$$

$$i_2 = -13 \text{ A}$$

$$i_1 = \frac{3i_2 + 22}{4}$$

$$\Rightarrow i_1 = \frac{-39 + 22}{4}$$

$$i_1 = -4.25 \text{ A}$$

$$i_3 = \frac{12 + 3 \times (-13)}{12}$$

$$= \frac{-27}{12}$$

$$= -2.25 \text{ A}$$

$$I_2 = I_1 + I_3 \quad - \textcircled{1}$$

KVL \Rightarrow


$$-E_1 + I_1 R_1 + I_2 R_2 - E_2 = 0 \quad + E_2 - I_2 R_2 - I_3 R_3 = 0$$

$$\Rightarrow -10 + 4I_1 + 3I_2 - 12 = 0 \quad \Rightarrow 12 - 3I_2 - 12I_3 = 0$$

$$\Rightarrow 4I_1 + 3I_2 = 22 \quad - \textcircled{2}$$

Mesh current Analysis

Steps:

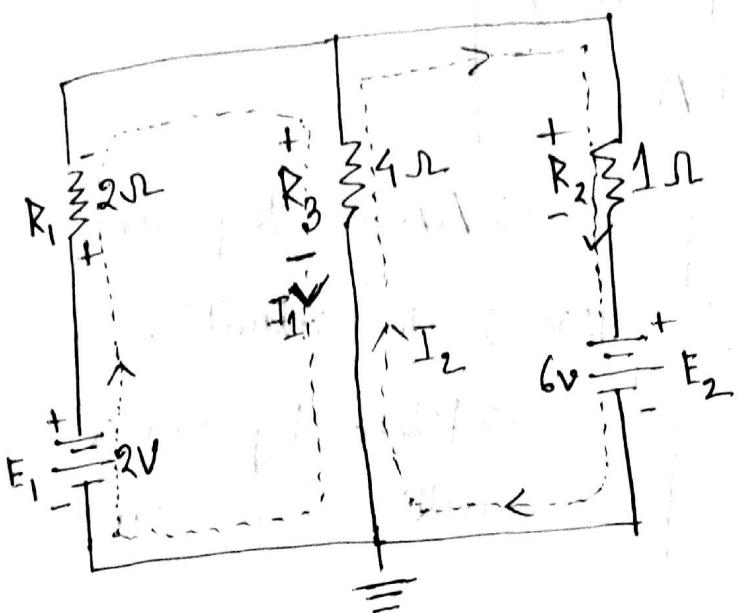

$$R_3 \rightarrow I = I_1 - I_2 \\ \text{or, } I_2 = I_1$$

1. Assign loop current to all independent loops in the clockwise direction.
2. Indicate polarities according to loop current.
3. Apply KVL to each loop in the clockwise direction.
4. Solve equations.

KVL

loop 1 :

$$+2V - 2 \cdot I_1 - 4(I_1 - I_2) = 0 \\ \Rightarrow 2V - 2I_1 - 4I_1 + 4I_2 = 0 \Rightarrow 6I_1 - 4I_2 = 2$$

Loop 2 :

$$-4(I_2 - I_1) - 1 \cdot I_2 - 6 = 0$$

$$\Rightarrow -4I_2 + 4I_1 - I_2 - 6 = 0$$

$$\Rightarrow 4I_1 - 5I_2 = 6$$

$$I_1 = -1A ; I_2 = -2A$$


$$\begin{aligned} & 6I_1 \nearrow 4I_2 \nearrow 2 \\ & 4I_1 - 5I_2 = 6 \\ & \cancel{4I_1} \cancel{- 5I_2 = 6} \end{aligned}$$

$$\text{Current for } R_3 \Rightarrow I_3 = I_1 - I_2$$

$$= -1 - (-2)$$

$$I_3 = I_2 + I_1$$


Super Mesh current Analyzing = 1 A.

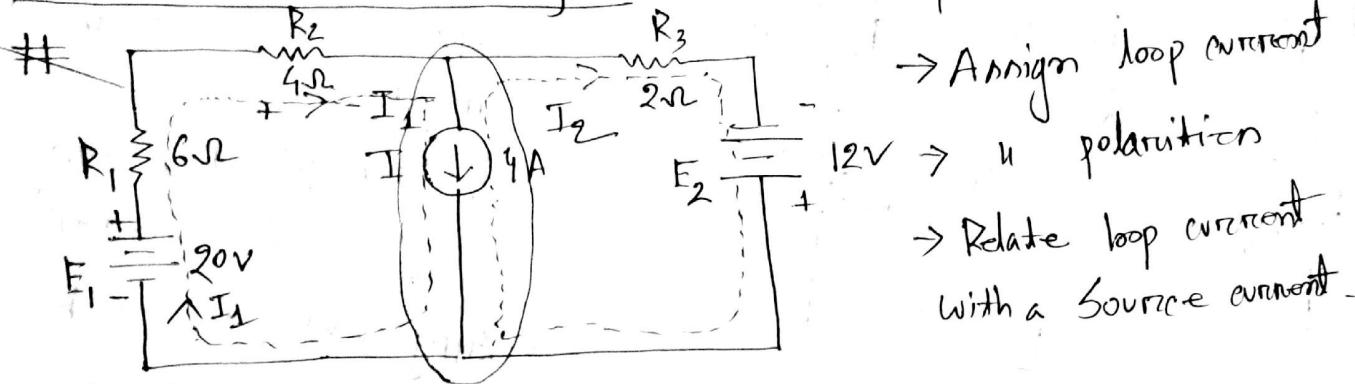


$$I_1 = 4 + I_2$$

$$+20V - 6I_1 - 4I_1 - 2I_2 + 12 = 0$$


Mid question : 2016 → I_4

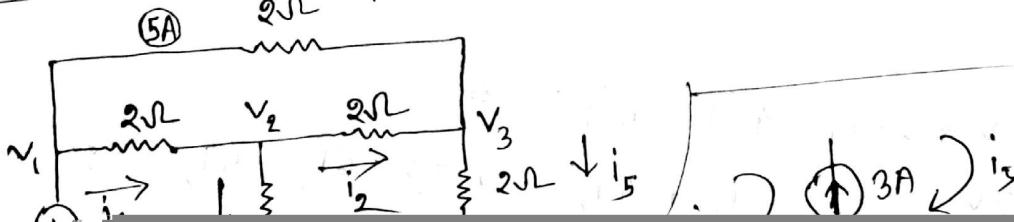

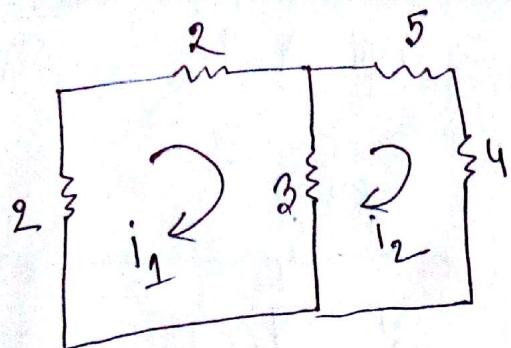



$$2i_1 + 2i_1 + 3i_1 - 3i_2 = 0$$

$$3i_2 + 5i_2 + 4i_2 - 3i_1 = 0$$

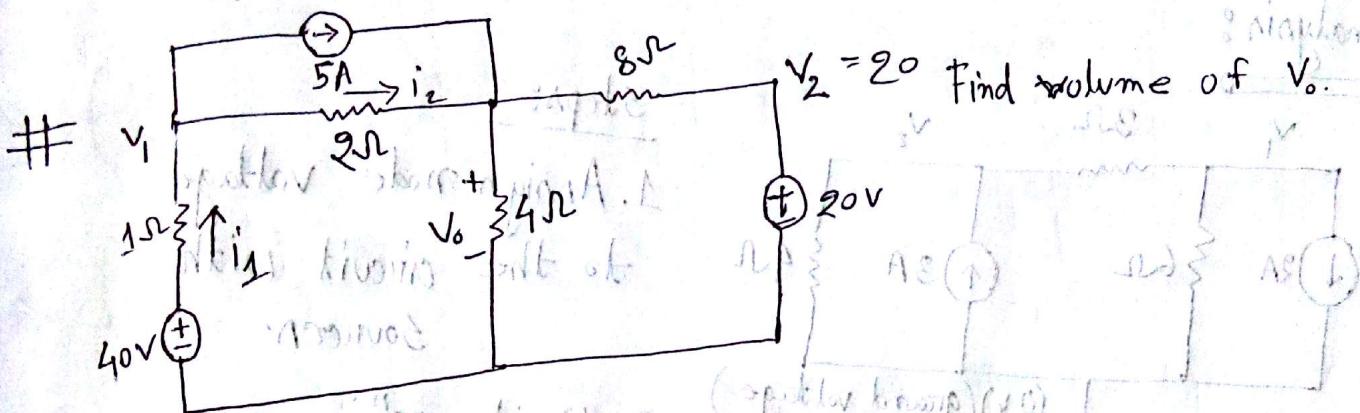

$$i_1 = 5 + i_2 \quad \text{--- (1)}$$
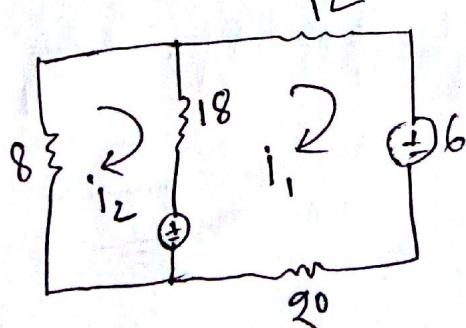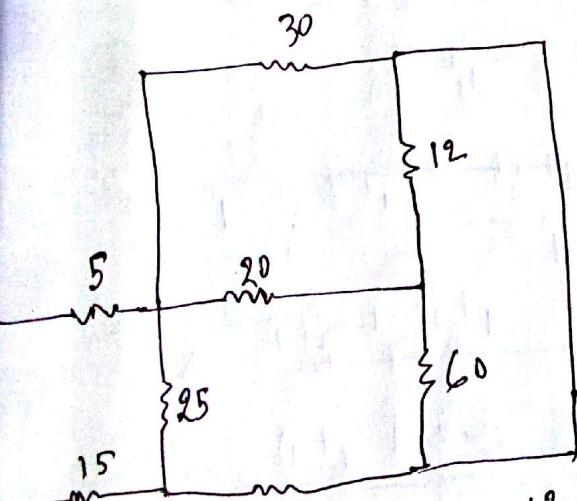
$$5 + i_2 = i_3 + i_4 \quad \text{--- (2)}$$



$$8i_2 + 18i_2 + 5 - 18i_1 = 0$$

$$18i_2 + 12i_1 + 6 - 18i_2 + 20i_1 = 0$$


Mesh + supernode - 1

Node + Supernode - 1

Thevenin
Superposition } - 1


others - 1

Nodal Analysis:

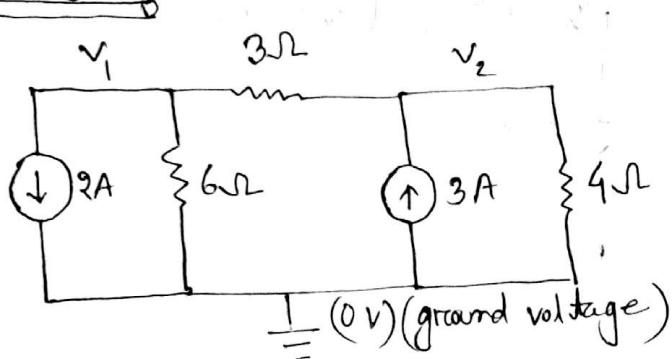


Steps:

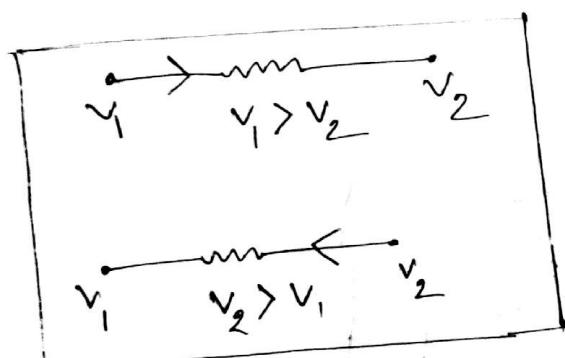1. Assign node voltage to the circuit with sources.
2. Write eqn.
3. Solve.



$$\underline{v_1} : \left(\frac{1}{3} + \frac{1}{6}\right)v_1 - \left(\frac{1}{3}\right)v_2 = -2A$$

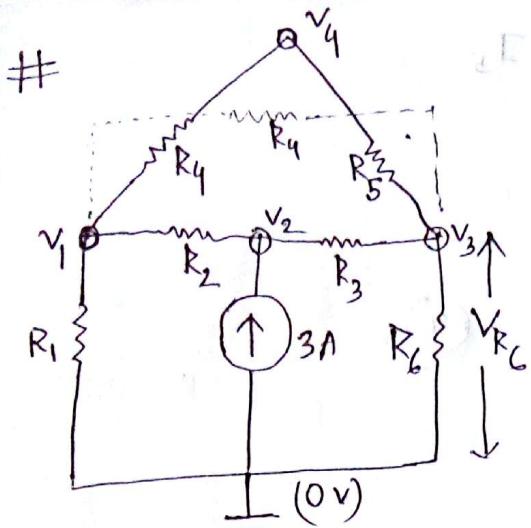
$$\underline{v_2} : \left(\frac{1}{3} + \frac{1}{4}\right)v_2 - \left(\frac{1}{3}\right)v_1 = +3A$$




$$v_1 : \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) v_1 - \left(\frac{1}{R_2} \right) v_2 - \left(\frac{1}{R_4} \right) v_3 = 0$$

$$v_2 : \left(\frac{1}{R_2} + \frac{1}{R_3} \right) v_2 - \left(\frac{1}{R_1} \right) v_1 - \left(\frac{1}{R_3} \right) v_3 = 0 + 3A$$
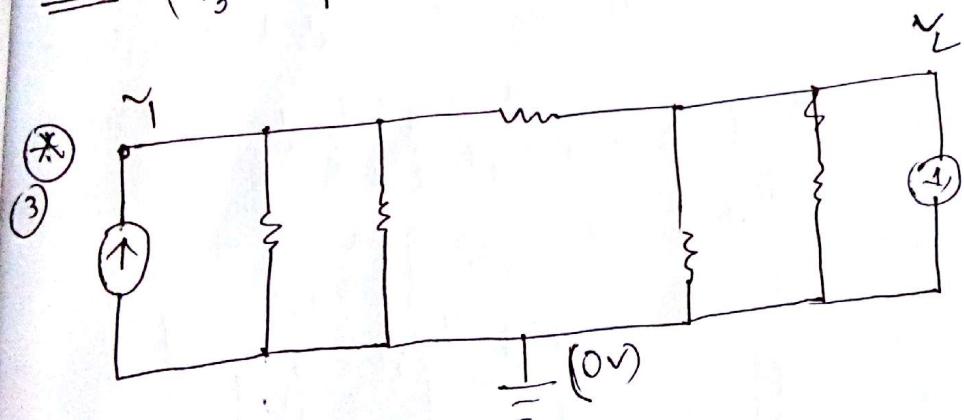
$$v_3 : \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_6} \right) v_3 - \left(\frac{1}{R_3} \right) v_2 - \left(\frac{1}{R_4} \right) v_1 = 0$$



Super Node :

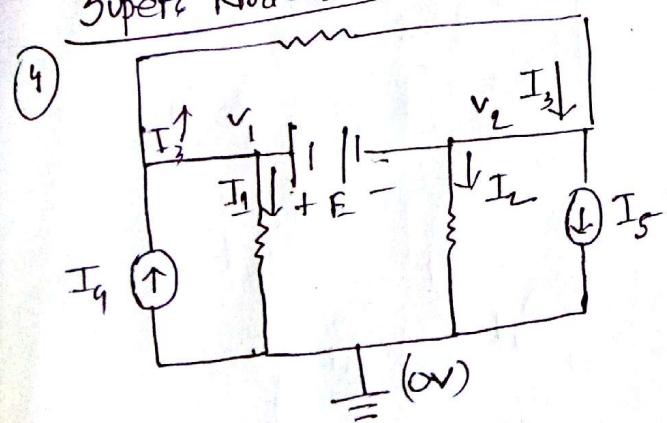

$\rightarrow v_1 \oplus v_2$

\rightarrow assign current.

\rightarrow relation betⁿ voltage source of nodal analysis.

$$E = v_1 - v_2$$


$$v_1 - v_2 = E \quad (1)$$

$$KCL \Rightarrow I_a + I_3 = I_3 + I_1 + I_2 + I_5$$

$$\Rightarrow I_a = I_1 + I_2 + I_5$$

$$I_1 + I_2 = 2$$
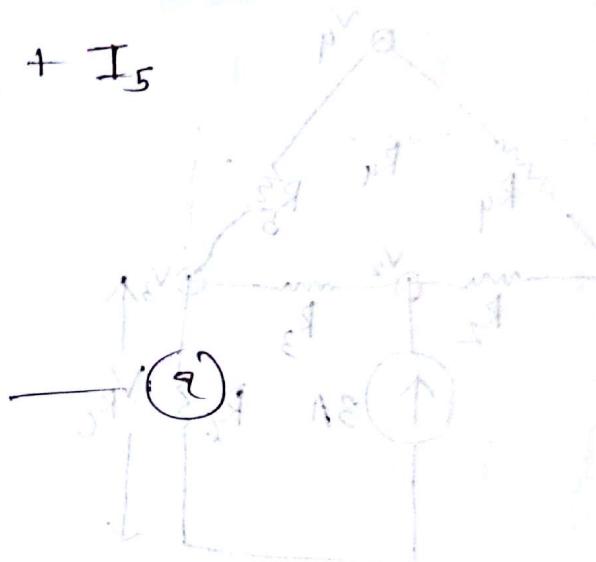
$$\left[\frac{V_1}{R_1} + \frac{V_2}{R_2} = 2 \right]$$



$$V_1 + V_2 + V_3 + V_4 = V_{total}$$

$$V_{total} = V_1 + V_2 + V_3 + V_4$$

X



Y